

# Verilog HDL

---


## MODULES AND PORTS

# Reference

---

Verilog HDL: A Guide to Digital Design  
and Synthesis, 2e, Samir Palnitkar

**Chapters 4**

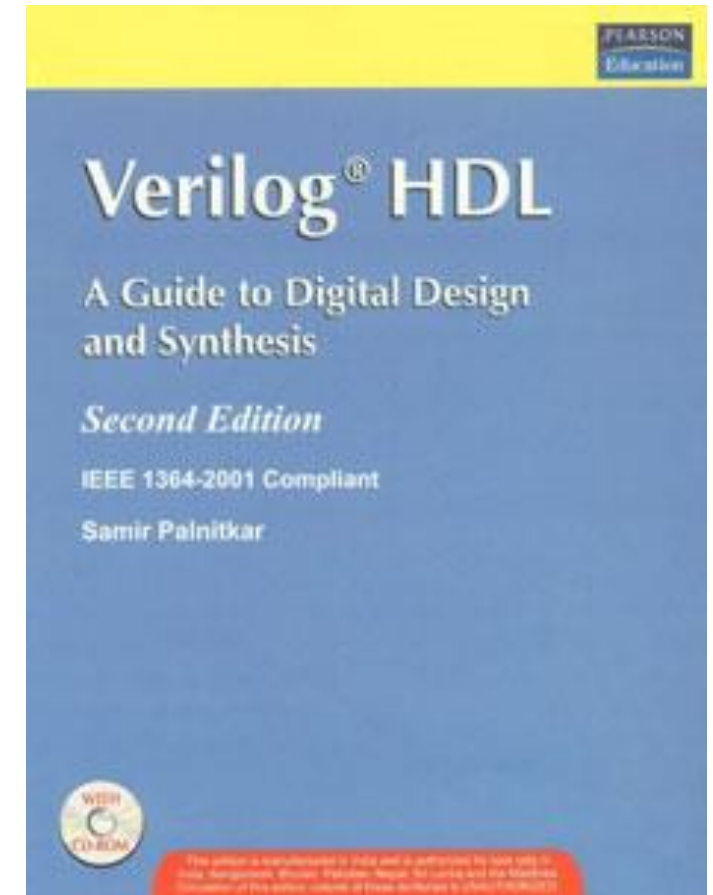


# Verilog Modules

---

- So far we looked at how modules are defined and instantiated.
- Now lets look at the internals of a module.

# Components of a module : an example

---

 

An SR Latch

# Components of a module : an example

---

```
// Module name and port list
// SR_latch module
module SR_latch(Q, Qbar, Sbar, Rbar);

    //Port declarations
    output Q, Qbar;
    input Sbar, Rbar;

    // Instantiate lower-level modules // In this case,
    // instantiate Verilog primitive nand gates // Note, how
    // the wires are connected in a cross-coupled fashion.
    nand n1(Q, Sbar, Qbar);
    nand n2(Qbar, Rbar, Q);

    // endmodule statement
endmodule
```

# Components of a module : an example

---

```
// Module name and port list : Stimulus module
module Top;
    // Declarations of wire, reg, and other variables
    wire q, qbar; reg set, reset;

    // Instantiate lower-level modules. In this case, instantiate SR_latch
    // Feed inverted set and reset signals to the SR latch
    SR_latch m1(q, qbar, ~set, ~reset);

    initial // Behavioural block, initial
    begin
        $monitor($time, " set = %b, reset= %b, q= %b\n", set, reset, q);
        set = 0; reset = 0;
        #5 reset = 1;
        #5 reset = 0;
        #5 set = 1;
    end

    // endmodule statement
endmodule
```

# Ports / terminals

---

- Ports provide the interface by which a module can communicate with its environment.
  - For example, the input/output pins of an IC chip are its ports.
- The environment can interact with the module only through its ports.
- The internals of the module are not visible to the environment.
  - Provides flexibility to the designer : The internals of the module can be changed without affecting the environment as long as the interface is not modified.


# List of Ports

---

- A module definition contains an optional list of ports.
- If the module does not exchange any signals with the environment, there are no ports in the list.


 
# Example : I/O Ports for Top and Full Adder



- module *Top* is a top-level module
  - no communication with the environment
  - no ports
- The module *fulladd4* is instantiated below *Top*
  - Does addition for its environments and hence does communication
  - has ports

```
module fulladd4(sum, c_out, a, b, c_in); //Module with a list of ports
module Top; // No list of ports, top-level module in simulation
```

# Port declaration


---

- All ports in the list of ports must be declared in the module.

Verilog Keyword	Type of Port
input	Input port
output	Output port
inout	Bidirectional port

# Port declaration : an example

---

 


- Note that all port declarations are implicitly declared as wire in Verilog.

```
module fulladd4(sum, c_out, a, b, c_in);  
  
    //Begin port declarations section  
    output[3:0] sum;  
    output c_cout;  
    input [3:0] a, b;  
    input c_in;  
    //End port declarations section  
  
    ... <module internals> ...  
  
endmodule
```
 
# Connecting ports to external signals

- The signals to be connected must appear in the module instantiation in the same order as the ports in the port list in the module definition.



```
module Top; //Declare connection variables
    reg [3:0] A,B; reg C_IN;
    wire [3:0] SUM; wire C_OUT;
    //Instantiate fulladd4, call it fa_ordered.
    //Signals are connected to ports in order (by position)
    fulladd4 fa_ordered(SUM, C_OUT, A, B, C_IN);
    ... <stimulus> ...
endmodule

module fulladd4(sum, c_out, a, b, c_in);
    output[3:0] sum; output c_cout;
    input [3:0] a, b; input c_in;
    ... <module internals> ...
endmodule
```